

Batteries have internal resistance, so we write:

$$\Delta V - IR = \mathcal{E} - Ir - IR = 0.$$

Resistances in series:

$$R_{\text{tot}} = \sum_i R_i.$$

Resistances in parallel:

$$\frac{1}{R_{\text{tot}}} = \sum_i \frac{1}{R_i}.$$

Networks of resistors: Identify groups, combine, and continue to combine until you are left with one equivalent resistor.

## Kirchhoff's Circuit Rules:

(1) At any circuit junction,  $(\sum_i I_i)_{\text{in}} = (\sum_i I_i)_{\text{out}}$ .  
**Charge is conserved.**

(2) Around any circuit loop,  $(\sum_i \Delta V_i)_{\text{rises}} = (\sum_i \Delta V_i)_{\text{drops}}$ .  
**Energy is conserved.**



Guess a current direction. Then, look at the various loops in the circuit.

- if you loop with the current, then  $\Delta V < 0$  across any resistor.
- If you loop against the current, then  $\Delta V > 0$  across any resistor.
- If you loop with the current, then  $\Delta V = \mathcal{E}$  across any battery.
- If you loop against the current, then  $\Delta V = -\mathcal{E}$  across any battery.
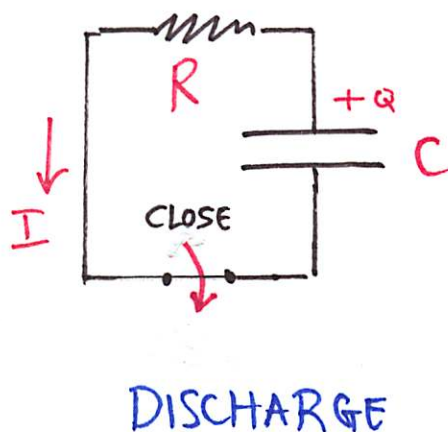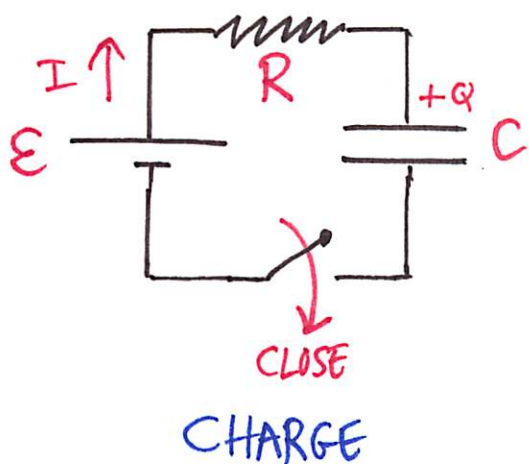
## RC Circuit:

Charging:  $q(t) = Q[1 - \exp(-t/RC)]$  where  $Q = C\mathcal{E}$ .

Discharging:  $q(t) = Q \exp(-t/RC)$  where  $Q = C\mathcal{E}$ .



Charging capacitor in RC circuit:

$$V_C = \mathcal{E} [1 - \exp(-t/RC)] \text{ and } V_R = \mathcal{E} \exp(-t/RC).$$

Discharging capacitor across R:

$$V_C = \frac{Q}{C} \exp(-t/RC), \quad I(t) = -\frac{Q}{RC} \exp(-t/RC)$$

$$\text{and } V_R = -\frac{Q}{C} \exp(-t/RC).$$